

FUTURE VISION BIE

One Stop for All Study Materials
& Lab Programs



Future Vision

By K B Hemanth Raj

Scan the QR Code to Visit the Web Page



Or

Visit : <https://hemanthrajhemu.github.io>

Gain Access to All Study Materials according to VTU,
CSE – Computer Science Engineering,
ISE – Information Science Engineering,
ECE - Electronics and Communication Engineering
& MORE...

Join Telegram to get Instant Updates: https://bit.ly/VTU_TELEGRAM

Contact: MAIL: futurevisionbie@gmail.com

INSTAGRAM: www.instagram.com/hemanthraj_hemu/

INSTAGRAM: www.instagram.com/futurevisionbie/

WHATSAPP SHARE: <https://bit.ly/FVBIESHARE>

CBCS SCHEME

USN

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

15EC63

Sixth Semester B.E. Degree Examination, June/July 2018 VLSI Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Discuss the working of nMOS enhancement mode transistor operation with neat diagrams. (06 Marks)
- b. Explain the CMOS inverter DC characteristics highlighting the regions of operation. (10 Marks)

OR

- 2 a. With neat diagrams discuss the nMOS fabrication process steps. (09 Marks)
- b. Explain the following :
(i) Channel length modulation
(ii) Noise Margin (07 Marks)

Module-2

- 3 a. Discuss the CMOS design style with a diagram. (05 Marks)
- b. Draw the stick diagram for the following using CMOS logic:
(i) $Y = A + B + C$ (ii) 2 i/p NAND gate (05 Marks)
- c. Discuss the different contact cuts with an example to each. (06 Marks)

OR

- 4 a. With a diagram derive an expression for sheet resistance and mention the R_s values of metal, p and n transistor channels for 5 μm technology. (05 Marks)
- b. Derive an equation for rise time and fall time with respect to CMOS inverter. (08 Marks)
- c. Draw the circuit and stick diagram for 2 i/p NOR gate using CMOS logic. (03 Marks)

Module-3

- 5 a. Explain the constant field, constant voltage scaling models with a diagram and scaling effect table. (06 Marks)
- b. Discuss the problems associated in VLSI design. How do you reduce them? (05 Marks)
- c. Discuss the different bus architectures. (05 Marks)

OR

- 6 a. Discuss the design of a 4-bit adder. (07 Marks)
- b. With relevant diagram discuss Manchester carry chain operation. (05 Marks)
- c. Explain the carry select adder with a diagram. (04 Marks)

Module-4

- 7 a. Discuss the programmable logic array with its structure and floor plan. (05 Marks)
- b. Discuss the architectural issues related to VLSI sub system design. (06 Marks)
- c. Discuss the design of Data selectors. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 8 a. Explain the architecture of field programmable gate array. (10 Marks)
- b. Discuss the FPGA abstractions with a diagram. (06 Marks)

Module-5

- 9 a. Explain three transistor DRAM with its diagram and stick diagram. (07 Marks)
- b. Discuss the ASM chart for JK flip flop with its NAND logic arrangement. (09 Marks)

OR

- 10 a. Explain logic verification process with its functional equivalence diagram. (06 Marks)
- b. Discuss the design for manufacturability. (06 Marks)
- c. Discuss the Ad-hoc testing. (04 Marks)

* * * * *